

Please check that this question paper contains <u>09</u> questions and <u>02</u> printed pages within first ten <i>minutes</i> .	
[Total No. of Questions: 09]	[Total No. of Pages: 02]
Uni. Roll No.	
Program: B.Tech. EE (Sem. 5th)	
MEASUREMENT and INSTRUMENTATION	
Subject Code: PCEE-112	
Paper ID: 16464	
Scientific Calculator is allowed	
Time Allowed: 03 Hours	Max. Marks: 60
Note:	
1)	Parts A and B are compulsory
2)	Part C has two questions Q8 and Q9 . Both are compulsory, but with internal choice.
3)	Any missing data may be assumed appropriately
Part – A [Marks: 02 each]	
Q1.	
a)	Define static sensitivity of an instrument. Also mention its unit.
b)	State any two differences between null type and deflection type instruments.
c)	Draw a labeled diagram depicting hysteresis loop.
d)	Mention any two transducers each for measurement of level and flow.
e)	How one can measure a current flowing through a live conductor without breaking the circuit?
f)	Full form of RTD and LVDT. What is their use?
Part – B [Marks: 04 each]	
Q2.	Can Galvanometer be used as a voltmeter and ammeter? If yes then explain with the diagram.
Q3.	A voltmeter having a sensitivity of $1000\Omega/V$ reads 100V on its 150V scale when connected across an unknown resistor in series with a milli-ammeter. When the milli-ammeter reads 5mA, calculate: a) apparent resistance of the unknown resistor b) actual resistance of the unknown resistor and c) error due to loading effect of the voltmeter.
Q4.	Draw a low voltage Schering bridge. Derive the equations for capacitance and dissipation factor.
Q5.	Enlist different types of control systems used in analog instruments. With a suitable diagram explain any two .
Q6.	What is the need of an instrumentation system. Draw the block diagram showing the functional elements of a typical instrumentation system.

Q7.	Explain the construction and operation of flux meter.
Part – C [Marks: 12 each]	
Q8.	Draw the equivalent circuit and phasor diagram of a current transformer. Derive the expressions for its ratio and phase angles. OR What is meant by CRO? Explain how we can measure frequency of a signal and phase angle between two waveforms by using this instrument.
Q9.	What is the principle of strain gauge? Derive the expression for a Guage factor of a given wire when stress 's' is applied to it. The wire has the following dimensions: Length=L, Area of cross-section=A, Diameter =D, before being strained. The material of the wire has a resistivity= ρ .
OR	
	Diagrammatically explain the constructional details of Electrodynamometer type wattmeter. Also derive the torque equation. Draw a Wein Bridge? Write the expression for frequency to be calculated.
